
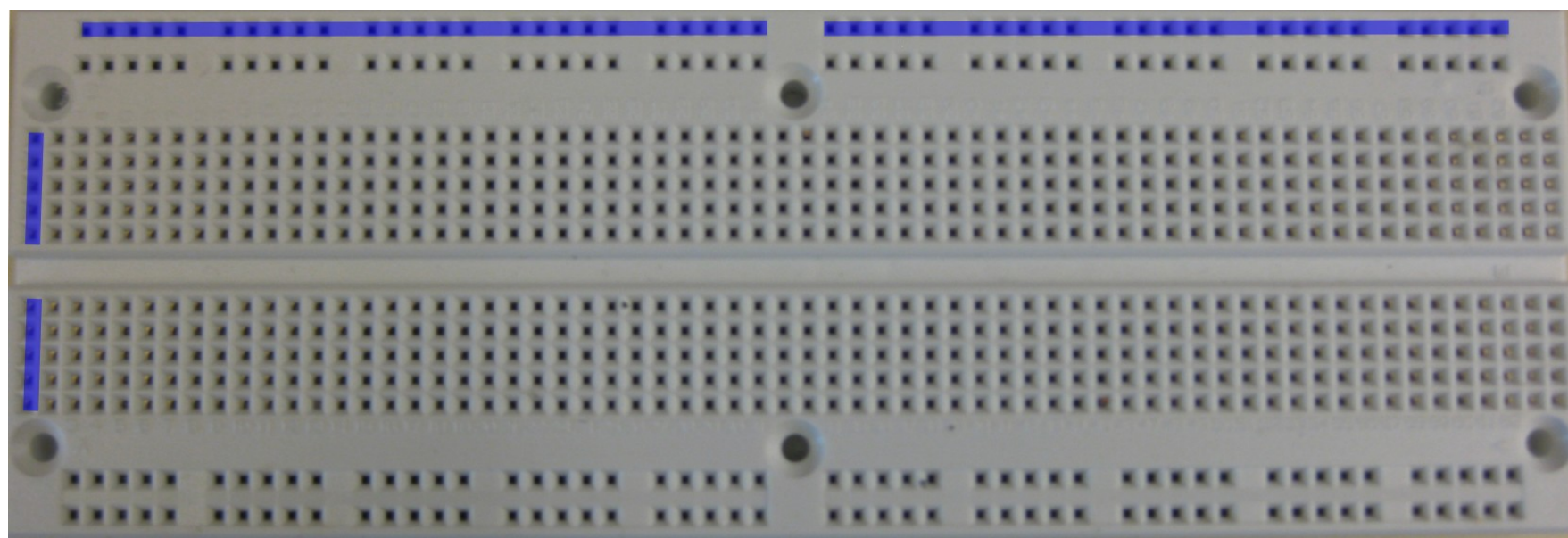


ECE 455 Orientation

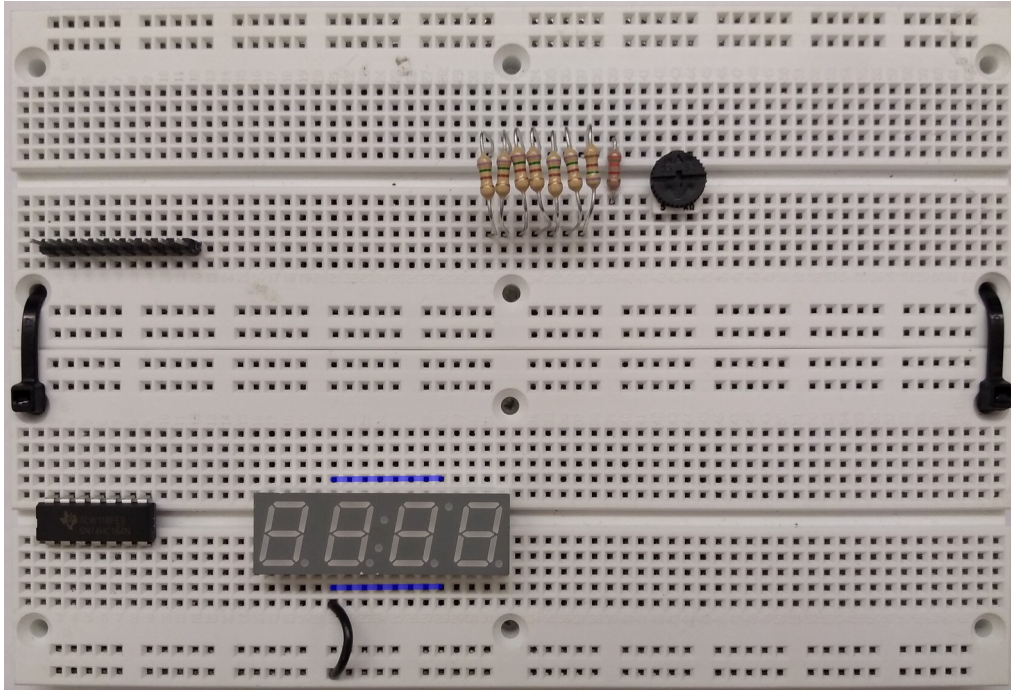- Circuit to build
- Building a circuit on a breadboard
- Using oscilloscope to make measurements
- Adding potentiometer to the circuit





Parts Being Used

74HC164 shift register

LTC-4727JR seven segment
common cathode display


750 Ohm resistors (7)

3.3K Ohm resistor


5K Potentiometer


10 pin header

6 jumper wires

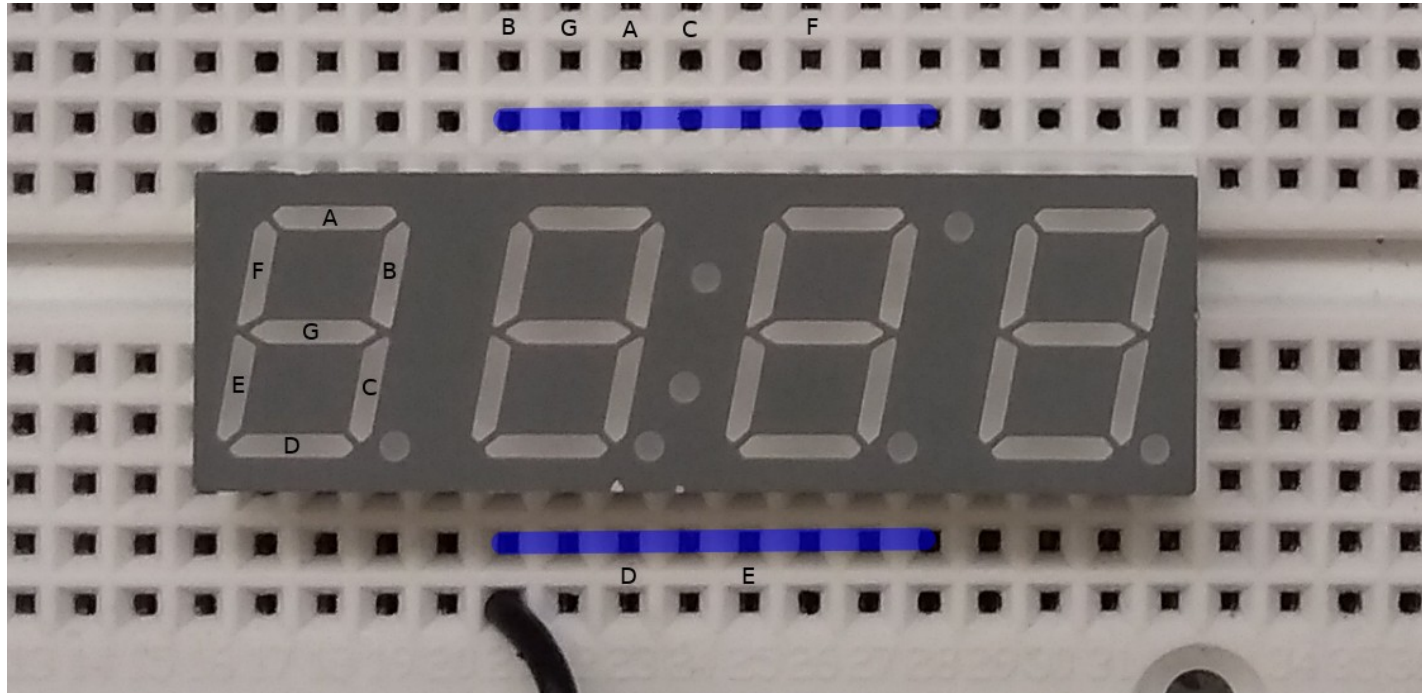


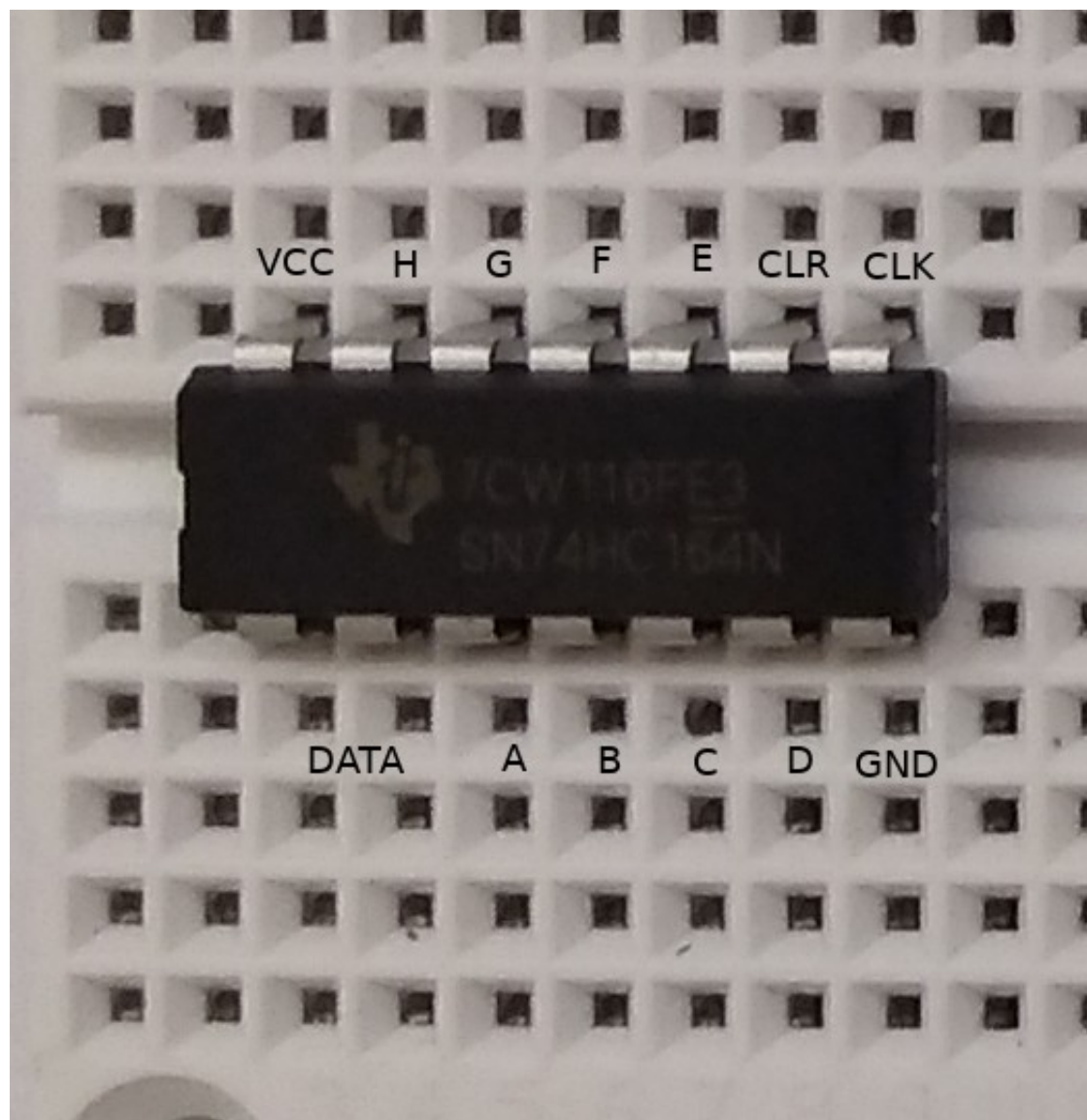A(Pin 13), B(Pin 16), C(Pin 13), D(Pin 3), E(Pin 5), F(Pin 11), G(Pin 14)



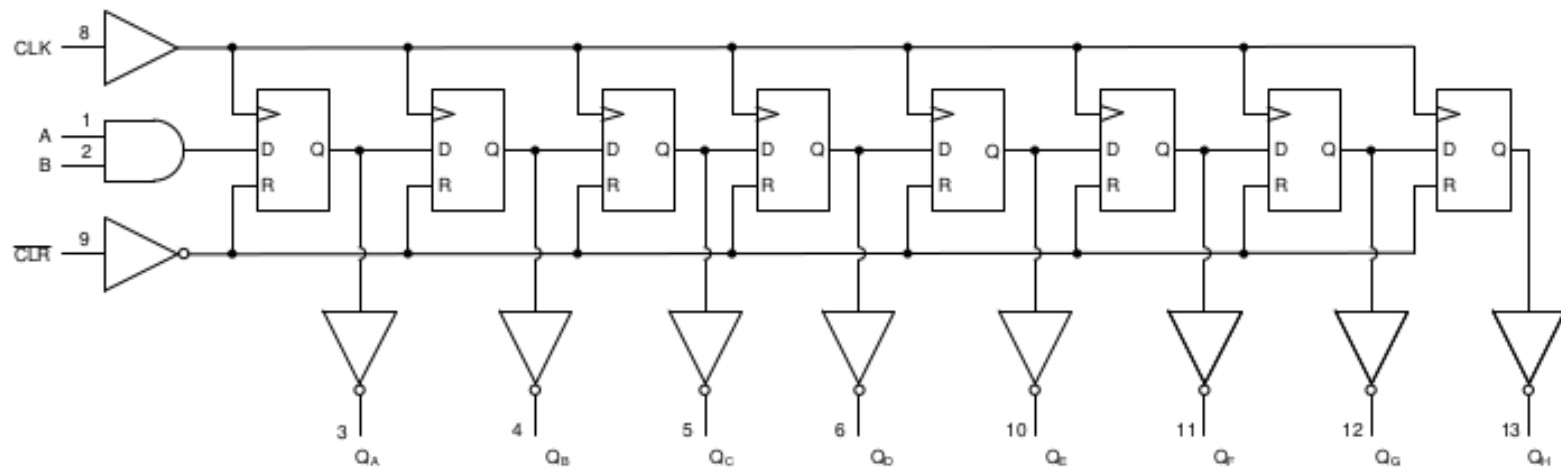



Functional Block Diagram

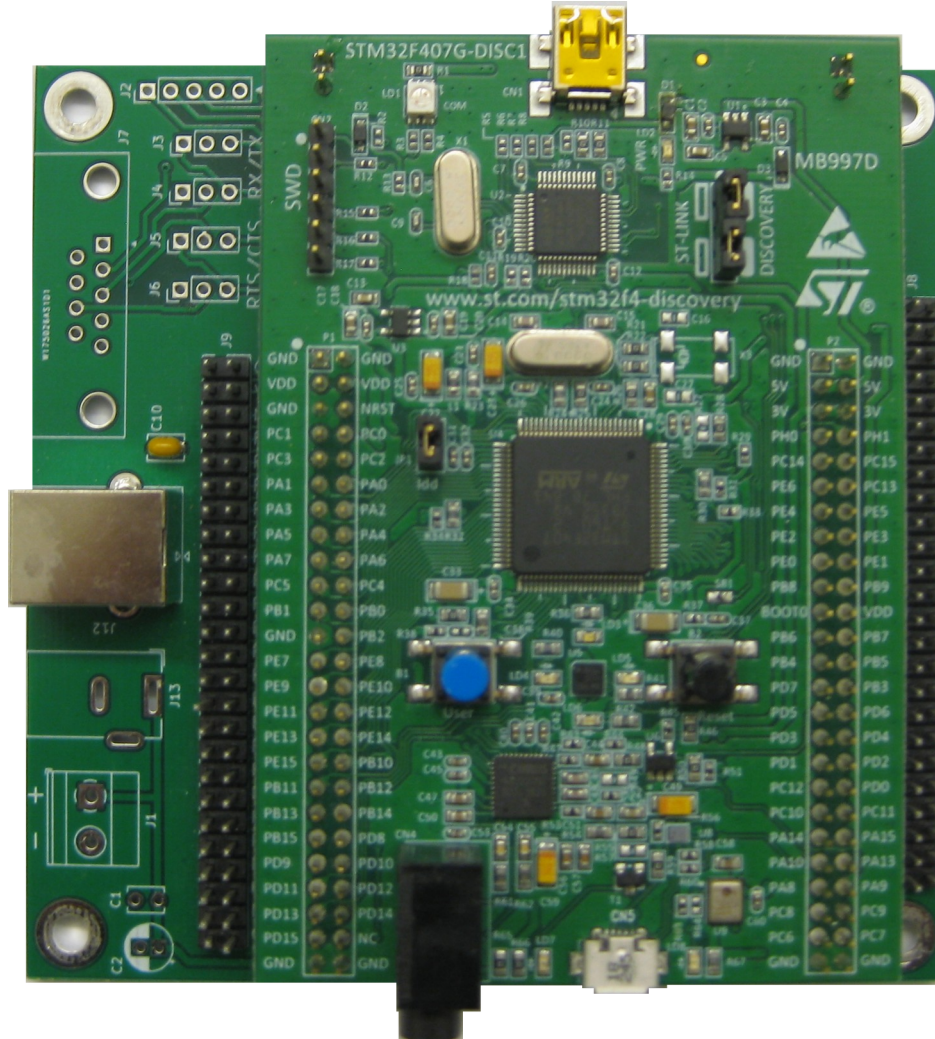

Signals Being Used

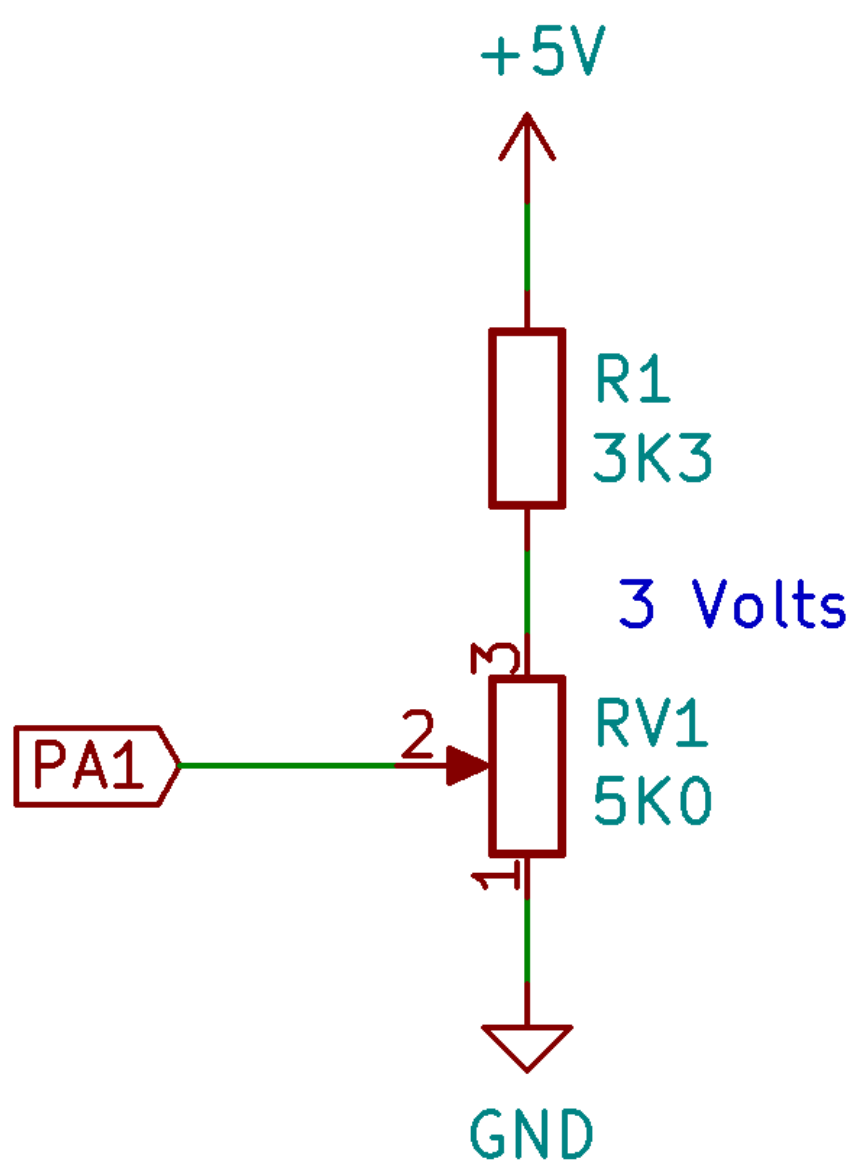PC6 Clear
PC8 Clock
PC9 Data
PA1 Potentiometer input
GND
5V



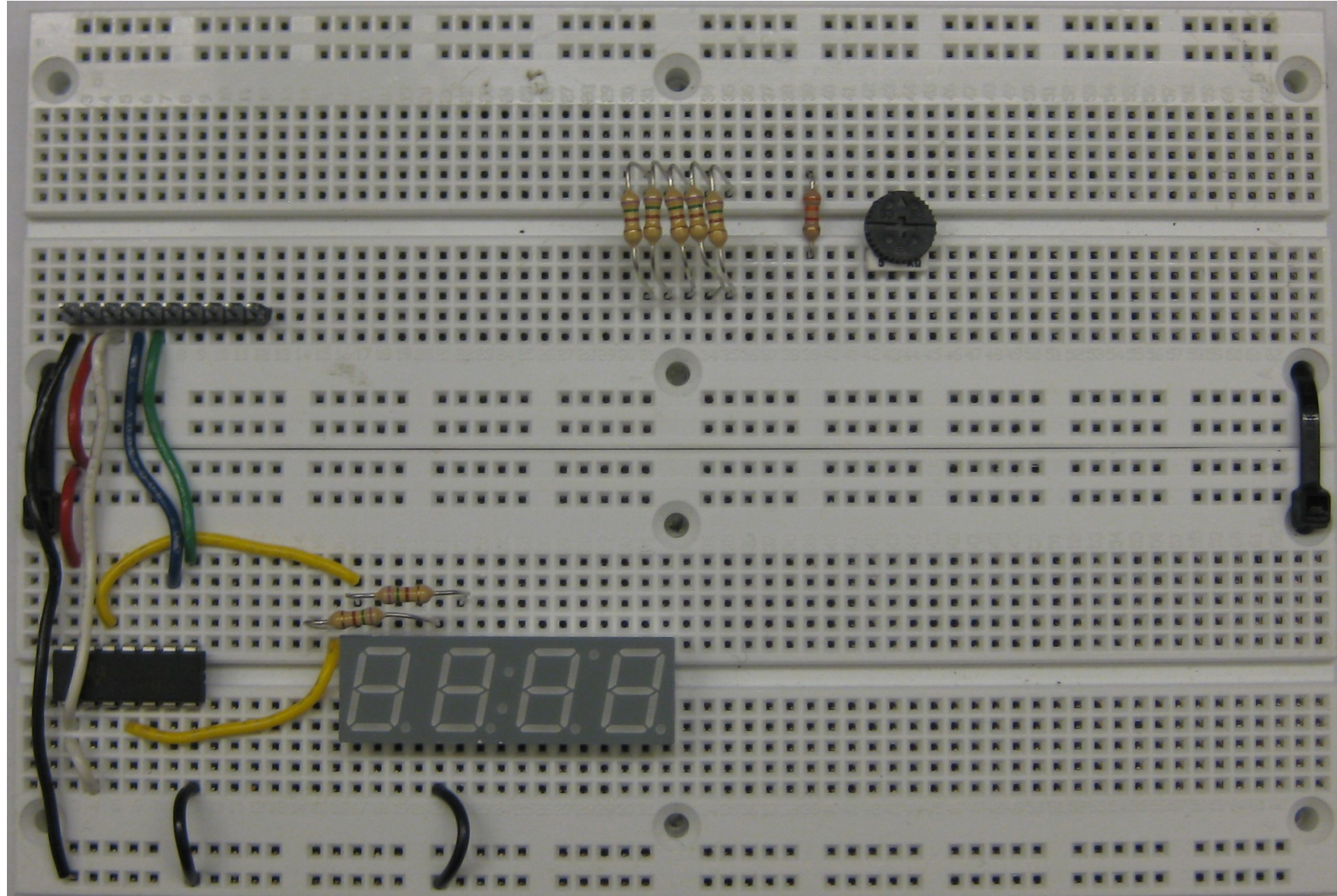

www.ece.uvic.ca/~brent/ece455/index.html